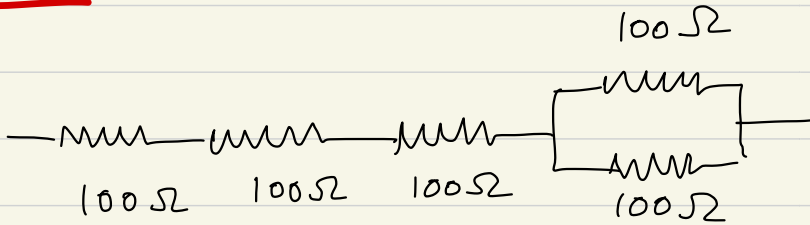


Problem 17

(a)




attempt (+1)


correct answer (+3)

(+4)

(b)

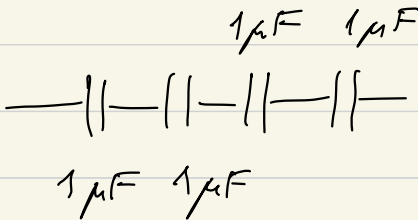


(c)

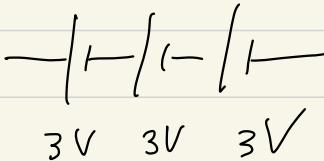

Problem 18

(a)

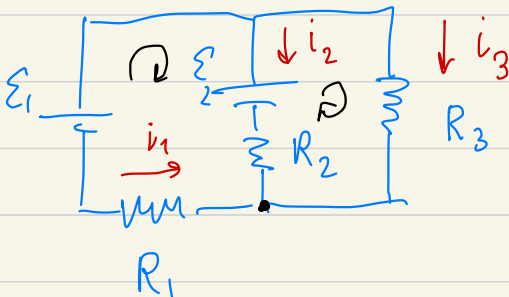

$$\begin{cases} i_1 + i_2 + i_3 = 0 \\ \varepsilon_1 - \varepsilon_2 - i_2 R_2 + i_1 R_1 = 0 \\ i_2 R_2 + \varepsilon_2 - i_3 R_3 = 0 \end{cases}$$

Exact solution : $i_3 = -i_1 - i_2 \Rightarrow$

(b)
(c)

$$\begin{cases} \mathcal{E}_1 - \mathcal{E}_2 - i_2 R_2 + i_1 R_1 = 0 & (1) \\ i_2 R_2 + \mathcal{E}_2 + (i_1 + i_2) R_3 = 0 & (2) \end{cases}$$

$$\mathcal{E}_1 - \mathcal{E}_2 - i_2 R_2 = -i_1 R_1 \Rightarrow$$

$$i_1 = \frac{i_2 R_2 + \mathcal{E}_2 - \mathcal{E}_1}{R_1}, \text{ plug into (2)}$$

$$i_2 R_2 + \mathcal{E}_2 + i_2 R_3 + \frac{i_2 R_2 + \mathcal{E}_2 - \mathcal{E}_1}{R_1} R_3 = 0$$

$$i_2 \left(R_2 + R_3 + \frac{R_2 R_3}{R_1} \right) + \mathcal{E}_2 + \frac{\mathcal{E}_2 - \mathcal{E}_1}{R_1} R_3 = 0$$

$$i_2 (R_2 R_1 + R_3 R_1 + R_2 R_3) + \mathcal{E}_2 R_1 + \mathcal{E}_2 R_3 - R_3 \mathcal{E}_1 = 0$$

$$i_2 = \frac{R_3 \mathcal{E}_1 - \mathcal{E}_2 R_3 - \mathcal{E}_2 R_1}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

0


Plugging values:

$$i_2 = -0.012 \text{ A}$$

$$i_1 = -0.010 \text{ A}$$

$$i_3 = 0.022 \text{ A}$$

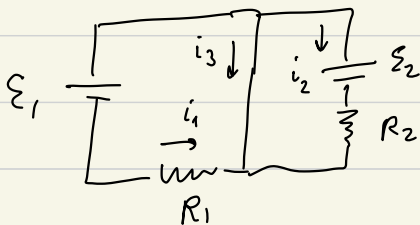Fast way: R_3 is essentially a short, so we can re-draw the circuit as



$$i_1 = -\frac{\mathcal{E}_1}{R_1} = -\frac{10 \text{ V}}{1000 \Omega} = -0.010 \text{ A}$$

$$i_2 = -\frac{\mathcal{E}_2}{R_2} = -\frac{12 \text{ V}}{1000 \Omega} = -0.012 \text{ A}$$


$$\text{and } i_3 = -i_1 - i_2 = 0.022 \text{ A}$$

Other values:

$$i_2 = -0.6 \text{ A}, \quad i_1 = -4 \cdot 10^{-6} \text{ A},$$

$$i_3 = 0.6 \text{ A}$$

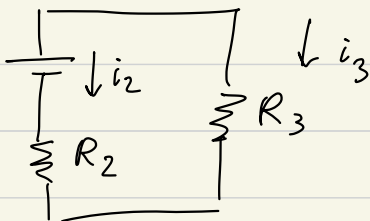
Fast way: R_3 is so big - it is a break, so: $i_1 = 0$



$$i_3 = -i_2 = \frac{\mathcal{E}_2}{R_2 + R_3} =$$

$$= \frac{12 \text{ V}}{20 \Omega} = 0.6 \text{ A}$$

Problem 19

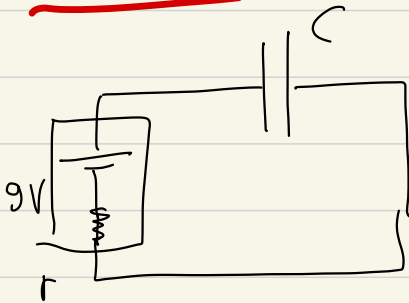

r - internal resistance

(b) Before C is charged, the current in the circuit is $\frac{\mathcal{E}}{r} = \frac{3V}{r} = 1A \Rightarrow r = 3\Omega$ (bad battery!)

(c) $C = \frac{\epsilon_0 A}{d}$ where A - surface area of lids, d - separation:

$$C = \frac{8.85 \cdot 10^{-12} \frac{F}{m} \cdot \pi \left(\frac{0.30m}{2} \right)^2}{0.013m} = 48.1 \cdot 10^{-12} F = 48.1 \text{ pF}$$

$$(d) \frac{CV^2}{2} = \frac{48.1 \cdot 10^{-12} F \cdot (3V)^2}{2} = 2.17 \cdot 10^{-10} J$$

Experiment 2

(2) Since the battery is disconnected Q - stays the same! It was $3V \cdot 48.1 \text{ pF} = 1.44 \cdot 10^{-10} \text{ C}$, so it stays the same.

Explanation (+1)
Correct answer (+1)

(f) C and V changed!

$$C = \frac{\epsilon_0 A}{d}, \text{ as } d \text{ increases by } \times 2 \Rightarrow$$

$$C_{\text{new}} = \frac{1}{2} C_{\text{old}}.$$

$$V = Ed = \frac{\sigma}{\epsilon_0} d \Rightarrow d \text{ increases by } \times 2,$$

$$V_{\text{new}} = 2V_{\text{old}}$$

$$\begin{aligned} PE &= \frac{CV^2}{2} \Rightarrow PE_{\text{new}} = \frac{C_{\text{new}} V_{\text{new}}^2}{2} = \\ &= \frac{1}{2} \frac{C_{\text{old}} \cdot 4V_{\text{old}}^2}{2} = \\ &= 2 \cdot \frac{C_{\text{old}} \cdot V_{\text{old}}^2}{2} = 2 PE_{\text{old}} \end{aligned}$$

$$\text{So } PE_{\text{new}} = 2 \cdot 2.17 \cdot 10^{-10} \text{ J} = 4.34 \cdot 10^{-10} \text{ J}$$

(g) The work goes into doubling the energy so

$$PE_{\text{old}} + \text{Work} = PE_{\text{new}} = 2PE_{\text{old}} \Rightarrow$$

$$\text{Work} = PE_{\text{old}} = 2.17 \cdot 10^{-10} \text{ J}$$

Problem 20

(a) The graph is difficult to read but it takes about 0.6 s for the voltage on the capacitor to increase to $\sim 66\%$ of the final value (1V),

$$\text{so } \tau_{RC} = 0.6 \text{ s} \quad (0.5 - 1 \text{ s is ok})$$

$$(b) \quad \tau_{RC} = RC = 0.6 \text{ s}$$

$$C = \frac{0.6 \text{ s}}{200 \Omega} = 3 \text{ mF}$$

(c) The capacitor is discharging, so

$$i = \frac{V}{R} e^{-\frac{t}{RC}} = \frac{1V}{200\Omega} e^{-\frac{0.5s}{0.6s}} \approx 2.17 \text{ mA}$$